

Computer Architecture (计算机体系结构)

Lecture 23 – Combinational Logic Blocks

2020-10-12



Lecturer Yuanqing Cheng


www.cadetlab.cn/~course

L19 Combinational Logic Blocks (1)

Cheng, fall 2020 © BUAA

Review

 - Use this table and techniques we learned to transform from 1 to another



L19 Combinational Logic Blocks (2)

Cheng, fall 2020 © BUAA


Today

- Data Multiplexors
- Arithmetic and Logic Unit
- Adder/Subtractor

L19 Combinational Logic Blocks (3)

Cheng, fall 2020 © BUAA

 Data Multiplexor (here 2-to-1, n-bit-wide)




L19 Combinational Logic Blocks (4)

Cheng, fall 2020 © BUAA

N instances of 1-bit-wide mux

How many rows in TT?

 

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$




L19 Combinational Logic Blocks (5)

Cheng, fall 2020 © BUAA

How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 


L19 Combinational Logic Blocks (6)

Cheng, fall 2020 © BUAA

4-to-1 Multiplexor?


How many rows in TT?

 

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$

Is there any other way to do it?


Hint: NCAA tourney!

 

Ans: Hierarchically!


Arithmetic and Logic Unit

 - Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR



when $S=00$, $R=A+B$
 when $S=01$, $R=A-B$
 when $S=10$, $R=A \text{ AND } B$
 when $S=11$, $R=A \text{ OR } B$

Our simple ALU

 

Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

Adder/Subtractor – One-bit adder LSB...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$

Adder/Subtractor – One-bit adder (1/2)...

	a_3	a_2	a_1	a_0
+	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0


a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 $s_i =$
 $c_{i+1} =$

L19 Combinational Logic Blocks (13)

Cheng, fall 2020 © BUAA

 Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

L19 Combinational Logic Blocks (14)

Cheng, fall 2020 © BUAA

N 1-bit adders \Rightarrow 1 N-bit adder

 

What about overflow?
Overflow = c_n ?


L19 Combinational Logic Blocks (15)

Cheng, fall 2020 © BUAA

What about overflow?

Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



Highest adder

- C_1 = Carry-in = C_{in} , C_2 = Carry-out = C_{out}
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op? C_{in} and $C_{out} \Rightarrow$ NO overflow!

- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!


L19 Combinational Logic Blocks (16)

Cheng, fall 2020 © BUAA

What about overflow?

Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 

Overflows when...


- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$

L19 Combinational Logic Blocks (17)

Cheng, fall 2020 © BUAA

Extremely Clever Subtractor

 

L19 Combinational Logic Blocks (18)

Cheng, fall 2020 © BUAA

Peer Instruction

- 1) Truth table for mux with 4-bits of signals has 2^4 rows
- 2) We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl

	12
a)	FF
b)	FT
c)	TF
d)	TT

Peer Instruction Answer

- 1) Truth table for mux with 4-bits of signals controls 16 inputs, for a total of 20 inputs, so truth table is 2^{20} rows... **FALSE**
 - 2) We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl ... **TRUE**
- 1) Truth table for mux with 4-bits of signals is 2^4 rows long
 - 2) We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl

	12
a)	FF
b)	FT
c)	TF
d)	TT

“And In conclusion...”

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter