
Computer Architecture

(计算机体系结构)

Lecture #16

State Elements: Circuits that Remember

2020-10-09



Yuanqing Cheng

www.cadetlab.cn/~courses

Review


- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types of circuits:**
 - **Stateless Combinational Logic (&,|,~)**
 - **State circuits (e.g., registers)**

Uses for State Elements

 - 1. As a place to store values for some indeterminate amount of time:**
 - Register files (like \$1-\$31 on the MIPS)
 - Memory (caches, and main memory)
- 2. Help control the flow of information between combinational logic blocks.**
 - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.

Accumulator Example

Why do we need to control the flow of information?




Want: $S=0;$
 for ($i=0; i<n; i++$)
 $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle.
- After n cycles the sum is present on S .

First try...Does this work?

 


Nope!


Reason #1... What is there to control the next iteration of the 'for' loop?

Reason #2... How do we say: 's=0'?

Second try...How about this?

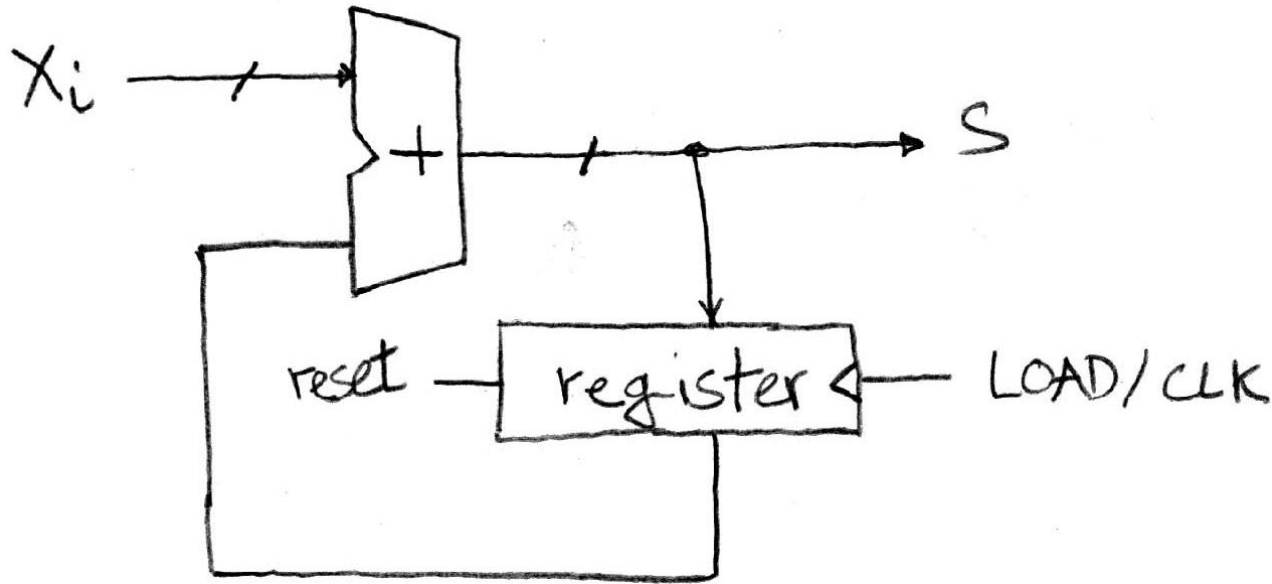


**Rough
timing...**

 

Register is used to hold up the transfer of data to adder.

Register Details...What's inside?

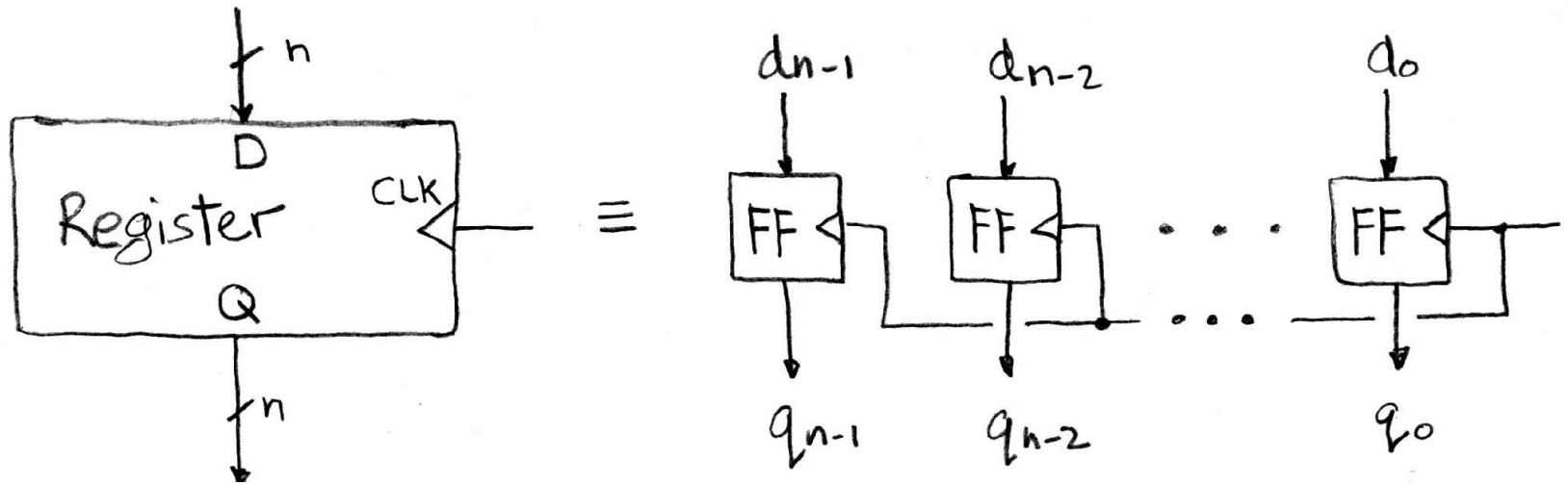


- n instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between 0,1
- D is “data”, Q is “output”
- Also called “d-type Flip-Flop”

What's the timing of a Flip-flop? (1/2)



- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”

 

- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”


- **Example waveforms:**

  

What's the timing of a Flip-flop? (2/2)



- Edge-triggered d-type flip-flop

- This one is “positive edge-triggered”

 


- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”


- Example waveforms (more detail):

  

 
Accumulator Revisited (proper timing 1/2)



 
- Reset input to register is used to force it to all zeros (takes priority over D input).
- S_{i-1} holds the result of the $i^{\text{th}}-1$ iteration.
- Analyze circuit timing starting at the output of the register.



 
Accumulator Revisited (proper timing 2/2)



 - reset signal shown.
- Also, in practice X might not arrive to the adder at the same time as S_{i-1}
- S_i temporarily is wrong, but register always captures correct value.
- In good circuits, instability never happens around rising edge of clk.



Maximum Clock Frequency

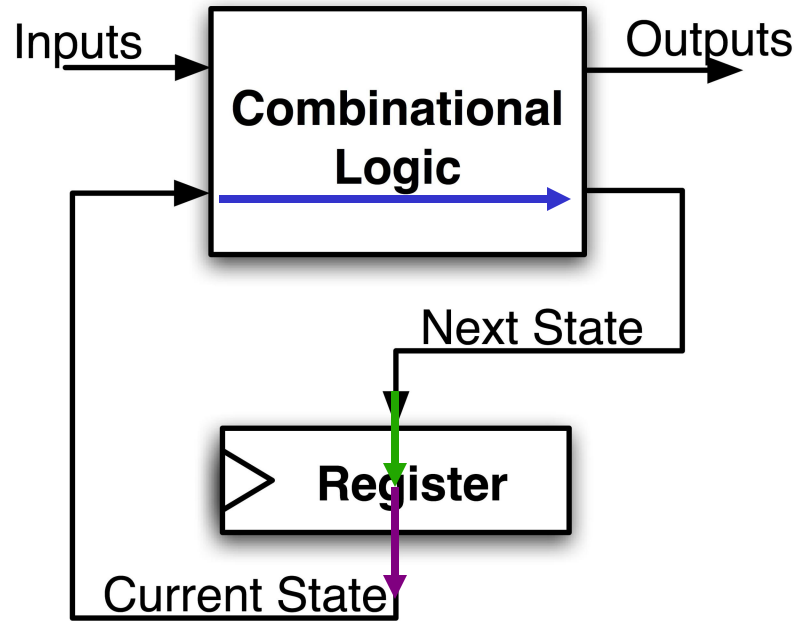


- What is the maximum frequency of this circuit?

$$\text{Max Delay} = \text{Setup Time} + \text{CLK-to-Q Delay} + \text{CL Delay}$$


Pipelining to improve performance

(1/2)

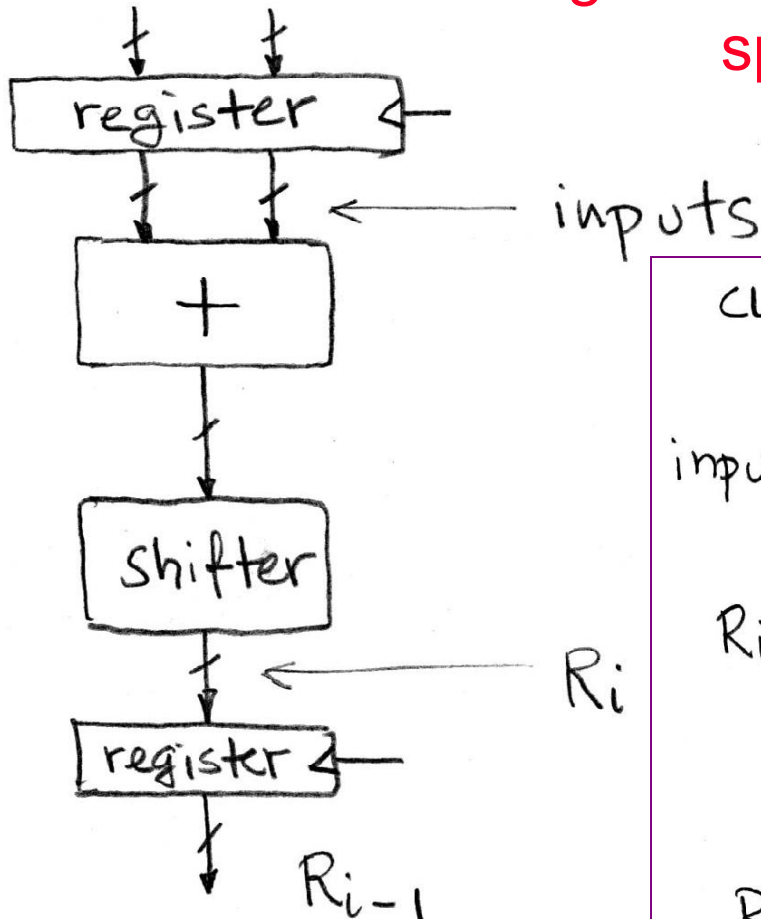Extra Register are often added to help speed up the clock rate.



Timing...

 


Note: delay of 1 clock cycle from input to output.

Clock period limited by propagation delay of adder/shifter.


Pipelining to improve performance

(2/2)

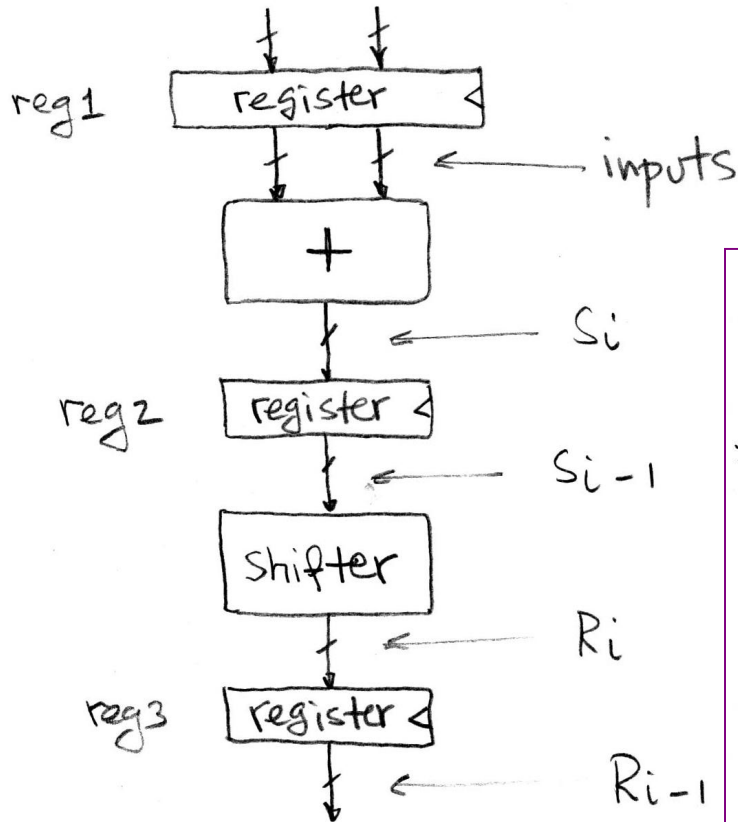

- Insertion of register allows higher clock frequency.
- More outputs per second.

Timing...

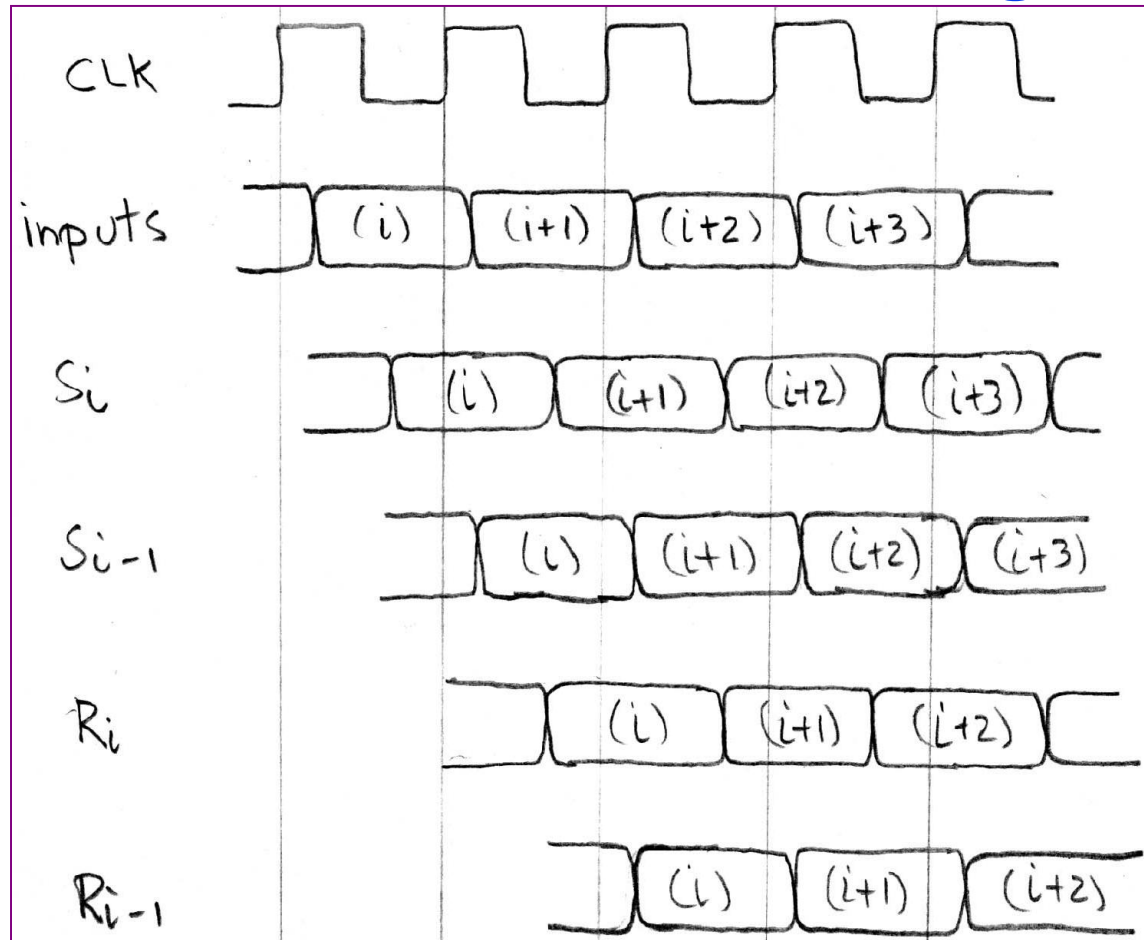


Recap of Timing Terms

- **Clock (CLK)** - steady square wave that synchronizes system
- **Setup Time** - when the input must be stable before the rising edge of the CLK
- **Hold Time** - when the input must be stable after the rising edge of the CLK
- **“CLK-to-Q” Delay** - how long it takes the output to change, measured from the rising edge
- **Flip-flop** - one bit of state that samples every rising edge of the CLK
- **Register** - several bits of state that samples on rising edge of CLK or on LOAD


Finite State Machines (FSM) Introduction

 - You have seen FSMs in other classes.
- Same basic idea.
- The function can be represented with a “state transition diagram”.
- With combinational logic and registers, any FSM can be implemented in hardware.




Finite State Machine Example: 3 ones...

 FSM to detect the occurrence of 3 consecutive 1's in the input.




Draw the FSM...

 


Assume state transitions are controlled by the clock:
on each clock cycle the machine checks the inputs and moves
to a new state and produces a new output...

Hardware Implementation of FSM

 
... Therefore a register is needed to hold the a representation of which state the machine is in. Use a unique bit pattern for each state.



+

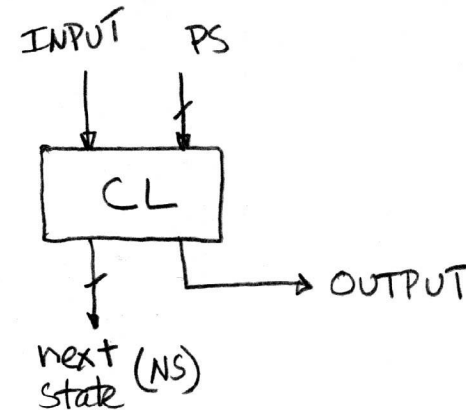


=

 

Combinational logic circuit is used to implement a function maps from *present state* and *input* to *next state* and *output*.

Hardware for FSM: Combinational Logic

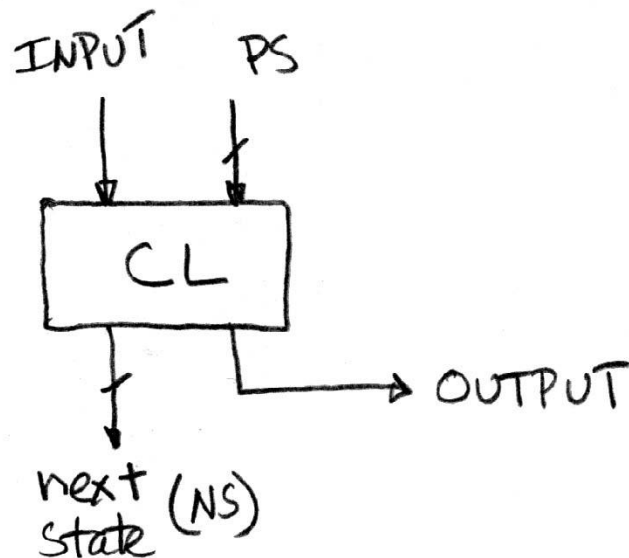
Next lecture we will discuss the detailed implementation, but for now can look at its functional specification, truth table form.



Truth table...

PS	Input	NS	Output
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

General Model for Synchronous Systems

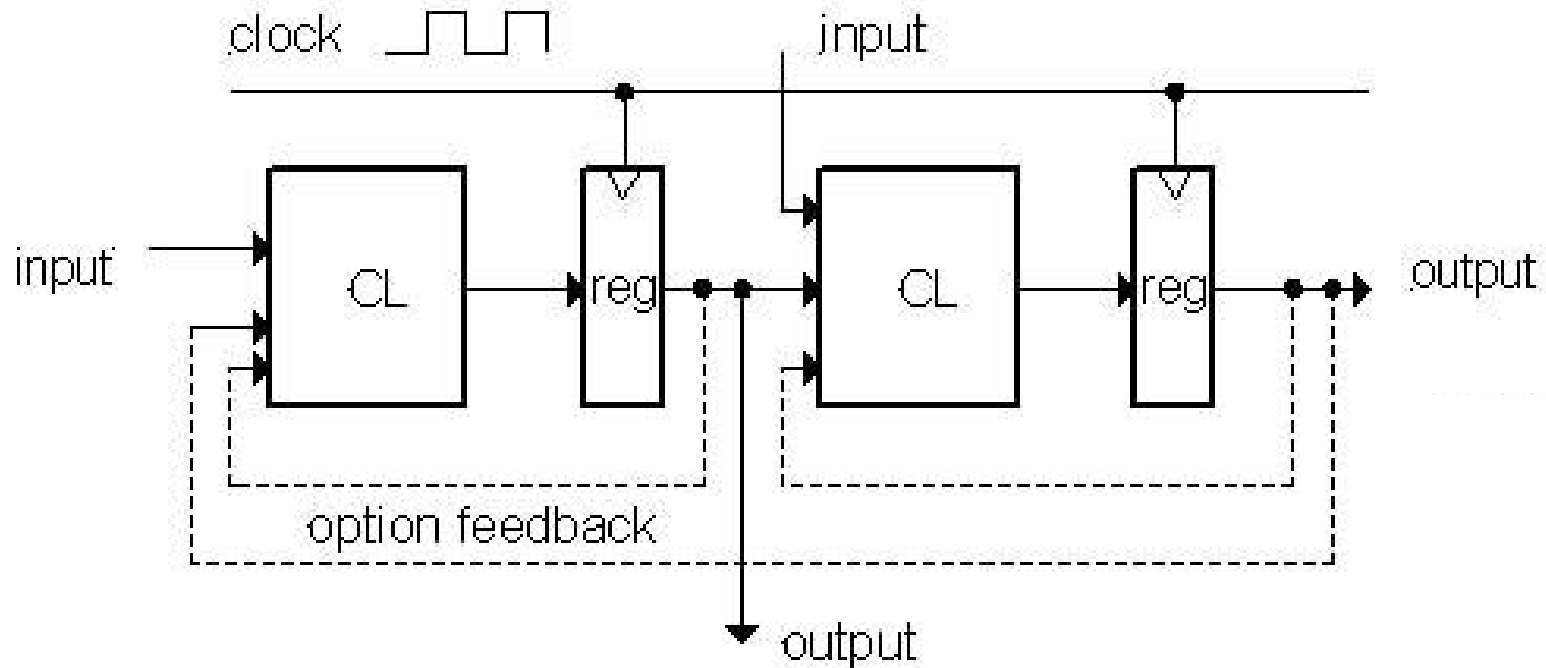

- Collection of CL blocks separated by registers.
- Registers may be back-to-back and CL blocks may be back-to-back.
- Feedback is optional.
- Clock signal(s) connects only to clock input of registers.

Peer Instruction

- A. HW feedback akin to SW recursion
- B. The period of a **usable synchronous circuit** is greater than the CLK-to-Q delay
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

	ABC
A:	FFF
B:	FTF
C:	TFF
D:	TTF
E:	TTT

Peer Instruction

- A. It needs 'base case' (reg reset), way to step from i to $i+1$ (use register + clock). **True!**
- B. If not, will loose data! **True!**
- C. How many states would it have? Say it's n . How does it know when $n+1$ bits have been seen? **False!**

- A. HW feedback akin to SW recursion
- B. The period of a **usable synchronous circuit** is greater than the CLK-to-Q delay
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

	ABC
A:	FFF
B:	FTF
C:	TFF
D:	TTF
E:	TTT

“And In conclusion...”

- **State elements are used to:**
 - **Build memories**
 - **Control the flow of information between other state elements and combinational logic**
- **D-flip-flops used to build registers**
- **Clocks tell us when D-flip-flops change**
 - **Setup and Hold times important**
- **We pipeline long-delay CL for faster clock**
- **Finite State Machines extremely useful**
 - **You'll see them again...**