

Lecture 22

Single-cycle CPU Control

2020-10-23

Lecturer Yuanqing Cheng
www.cadetlab.cn/~course




TSMC Sees HPC As Next Inflection Point




Review: A Single Cycle Datapath

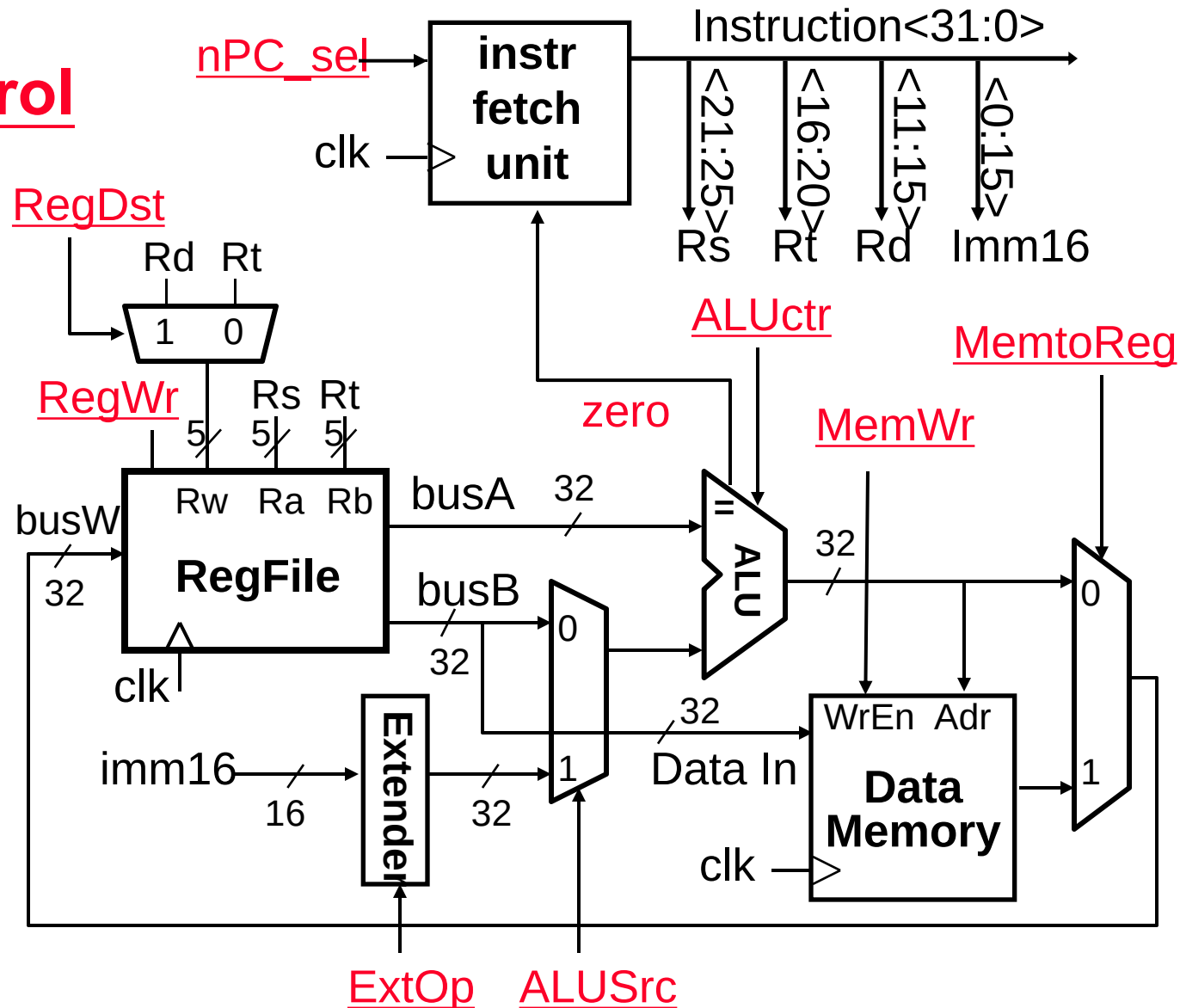- We have everything except control signals




Recap: Meaning of the Control Signals

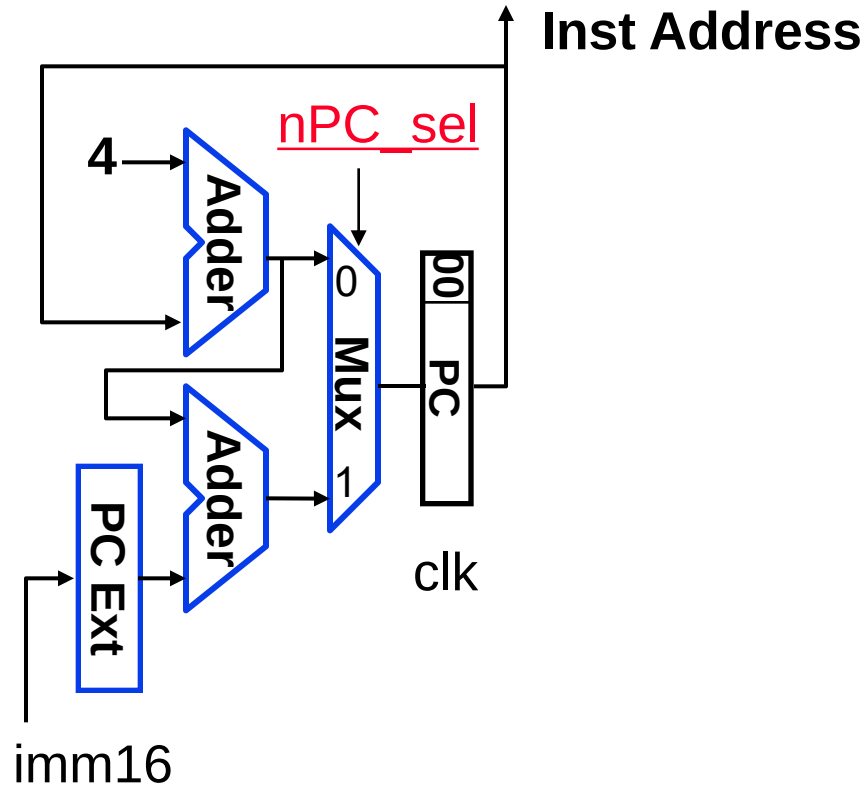- **nPC_sel:**
“n”=next
“+4” $0 \Rightarrow PC \leftarrow PC + 4$
“br” $1 \Rightarrow PC \leftarrow PC + 4 + \{ \text{SignExt(Imm16)}, 00 \}$
- Later in lecture: higher-level connection between mux and branch condition




Recap: Meaning of the Control Signals

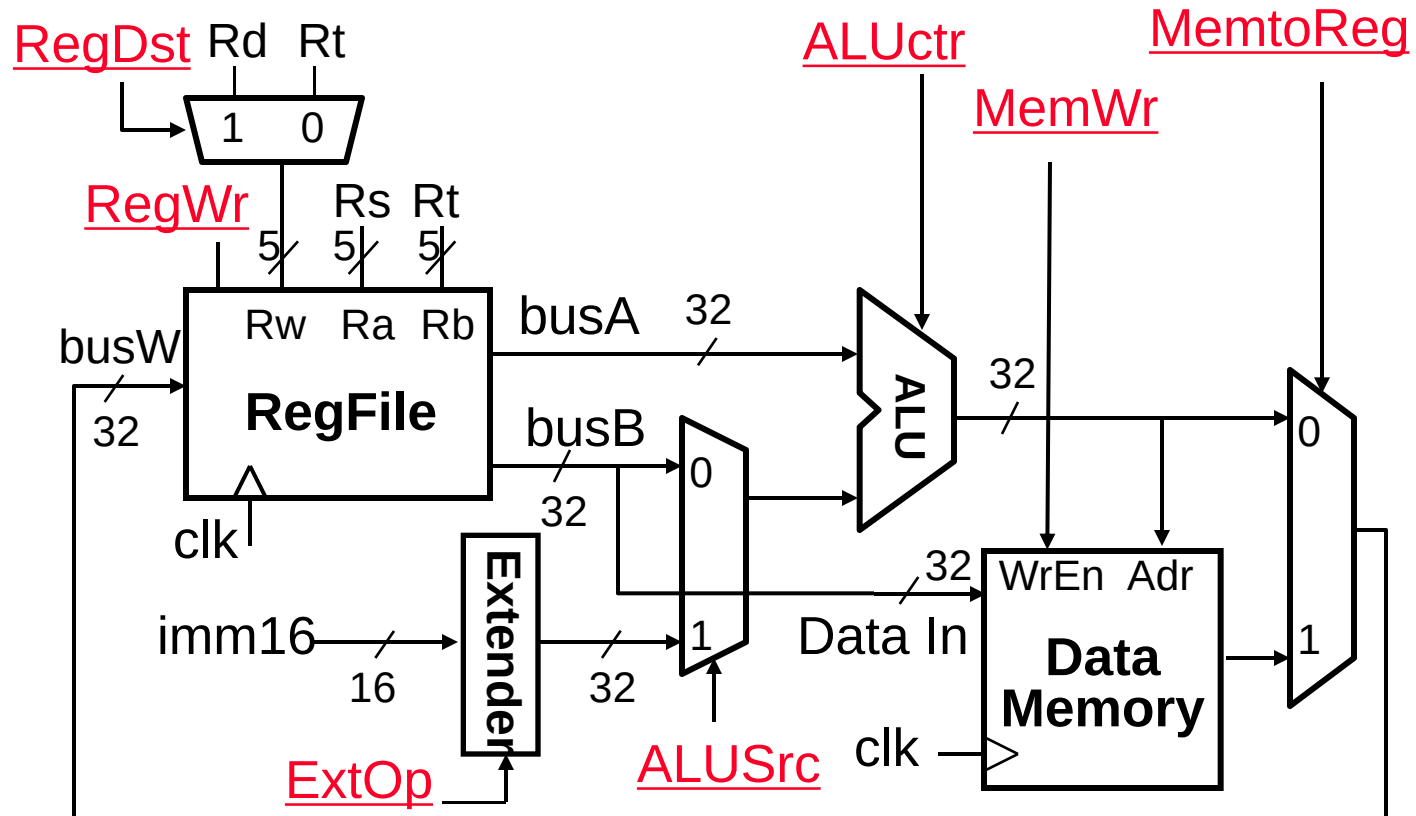- **ExtOp:** “zero”, “sign”
- **ALUsrc:** 0 \Rightarrow regB;
1 \Rightarrow immedi
- **ALUctr:** “ADD”, “SUB”, “OR”
- **MemWr:** 1 \Rightarrow write memory
- **MemtoReg:** 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst:** 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr:** 1 \Rightarrow write register



RTL: The Add Instruction

 


add rd, rs, rt

- **MEM[PC]** **Fetch the instruction from memory**
- **$R[rd] = R[rs] + R[rt]$** **The actual operation**
- **$PC = PC + 4$** **Calculate the next instruction's address**


Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory: $\text{Instruction} = \text{MEM}[\text{PC}]$

- same for all instructions

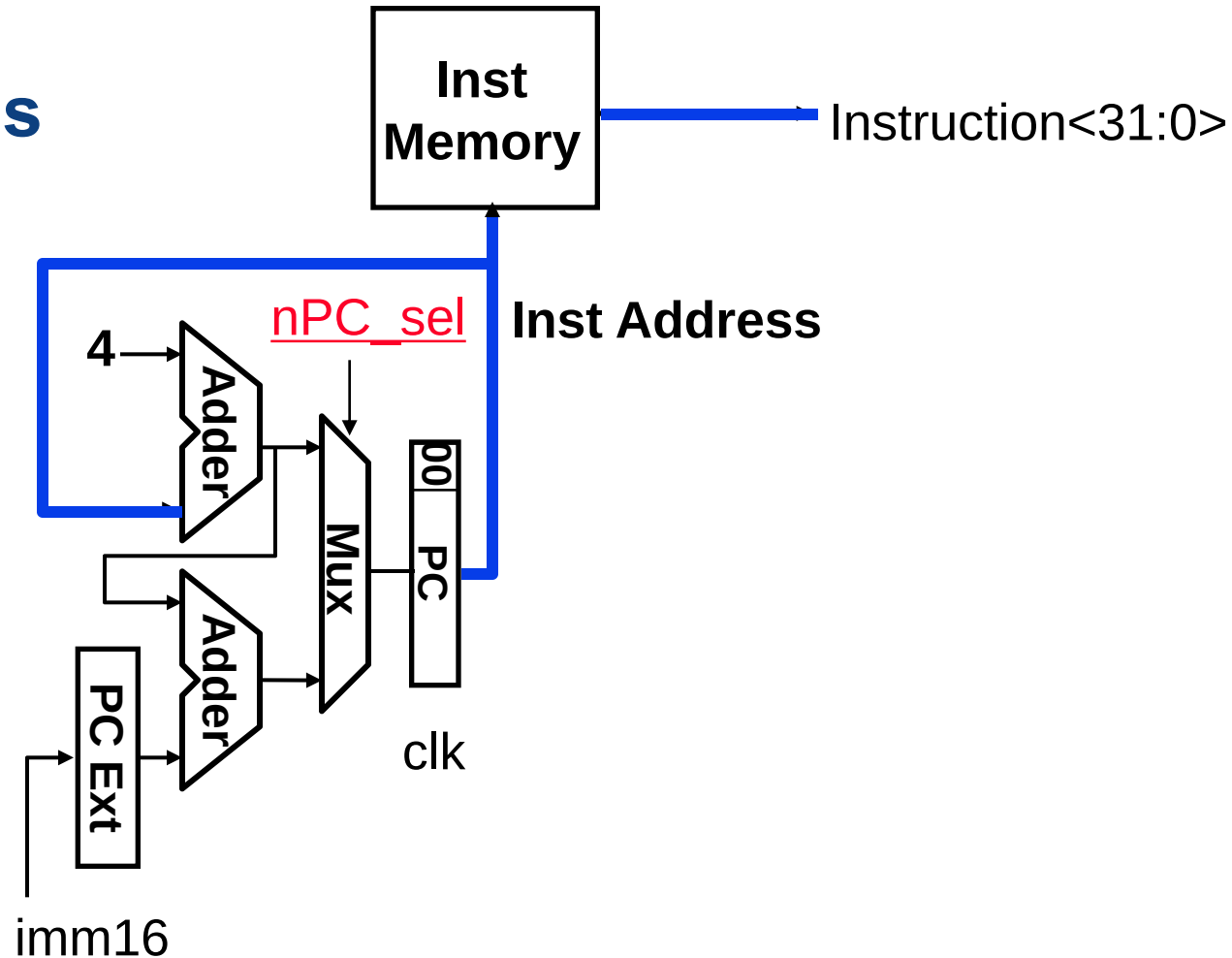


The Single Cycle Datapath during Add

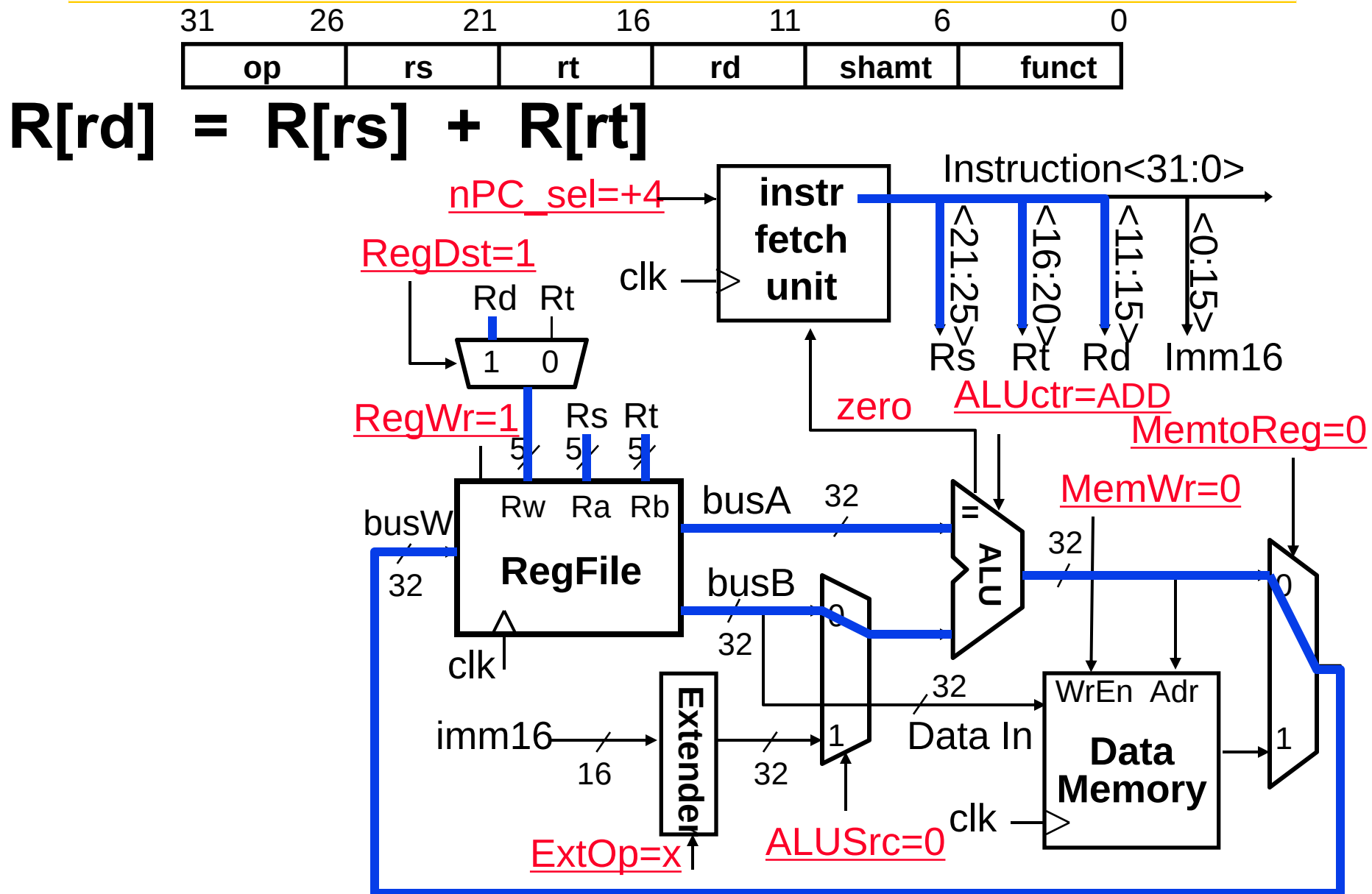


Instruction Fetch Unit at the End of Add

 
- **$PC = PC + 4$**
 - This is the same for all instructions except: Branch and Jump



 
Single Cycle Datapath during Or Immediate?



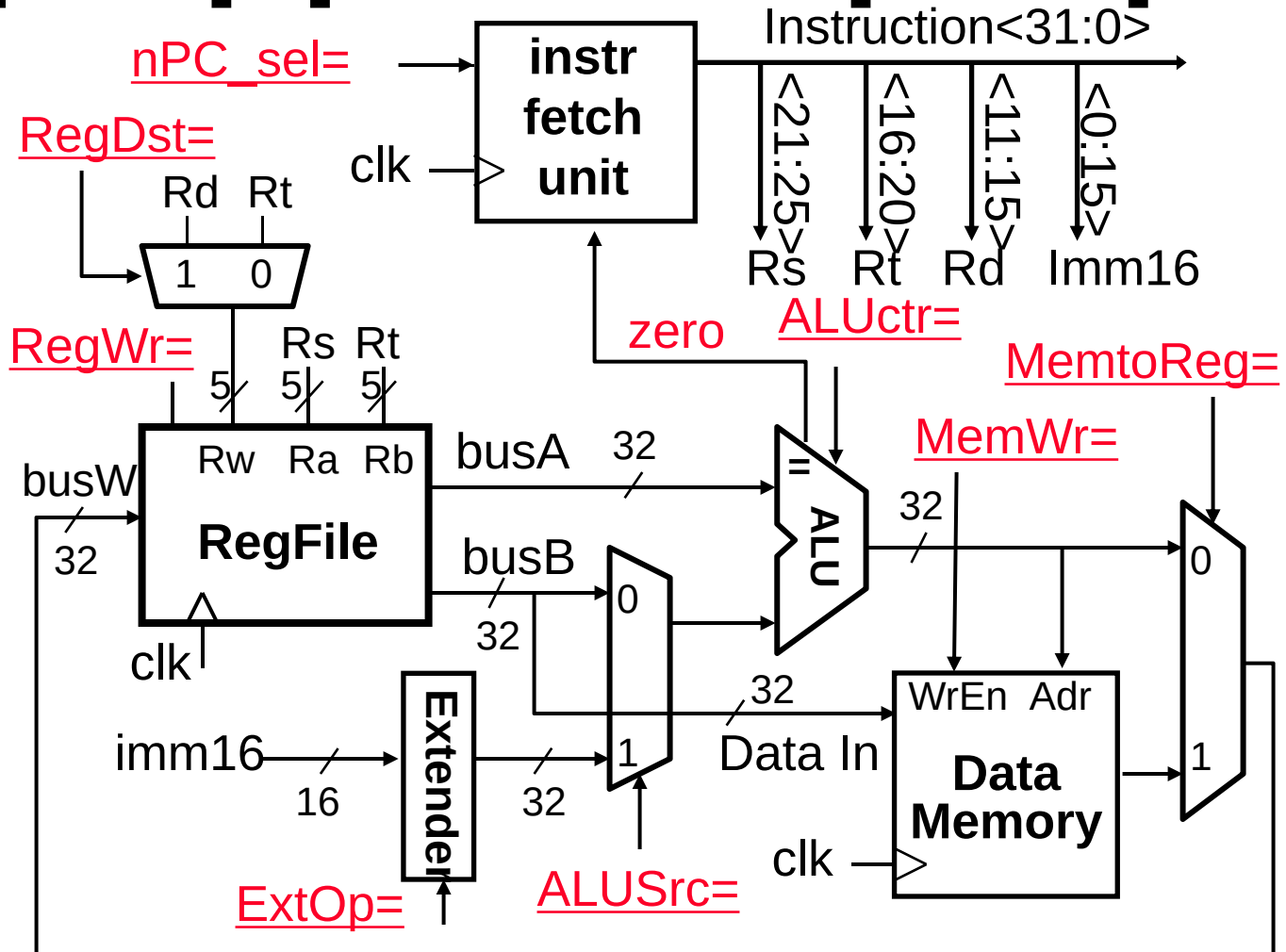
• $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$



 
Single Cycle Datapath during Or Immediate?



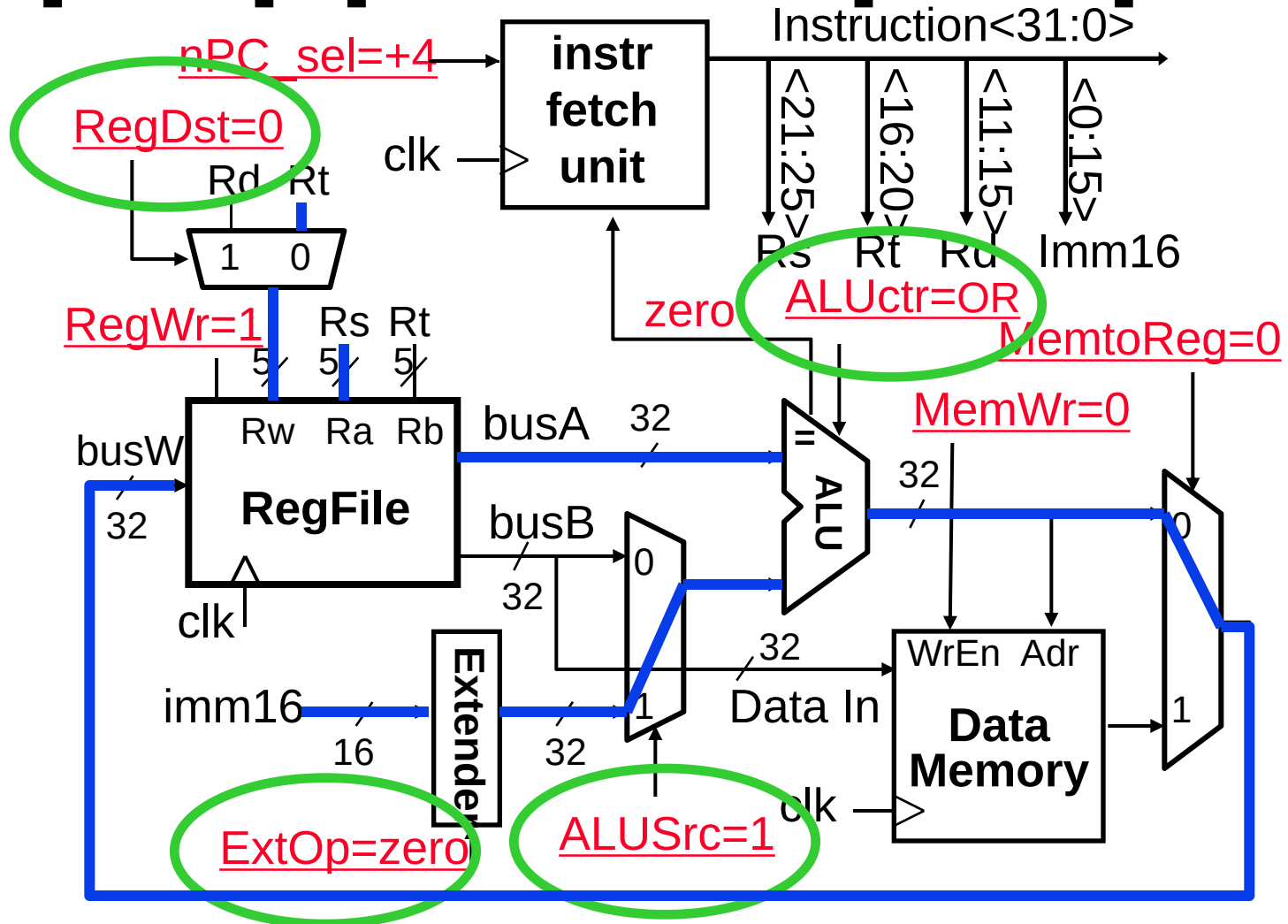
- $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




The Single Cycle Datapath during Load?

 

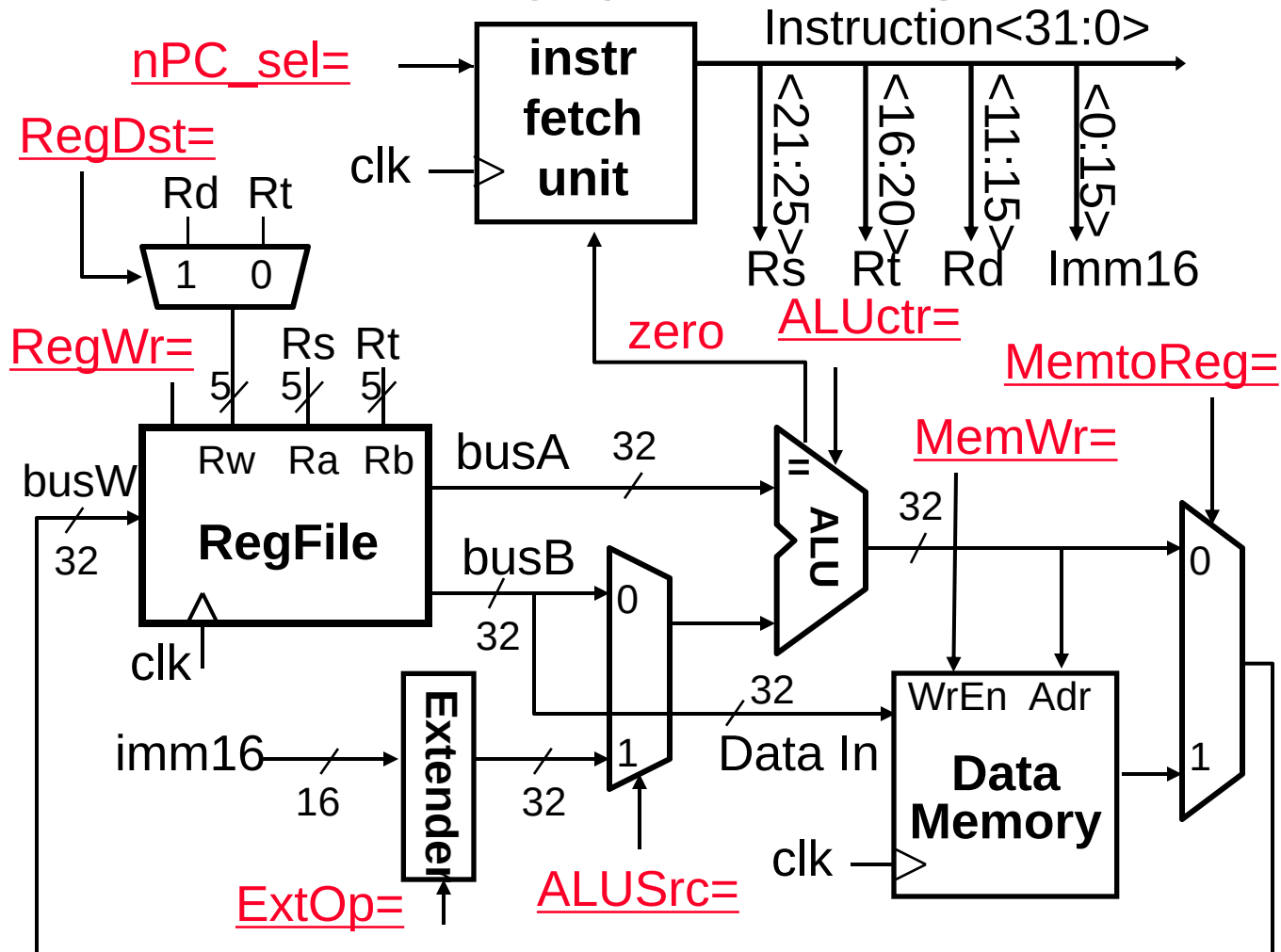
- $R[rt] = \text{Data Memory } \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Load

 

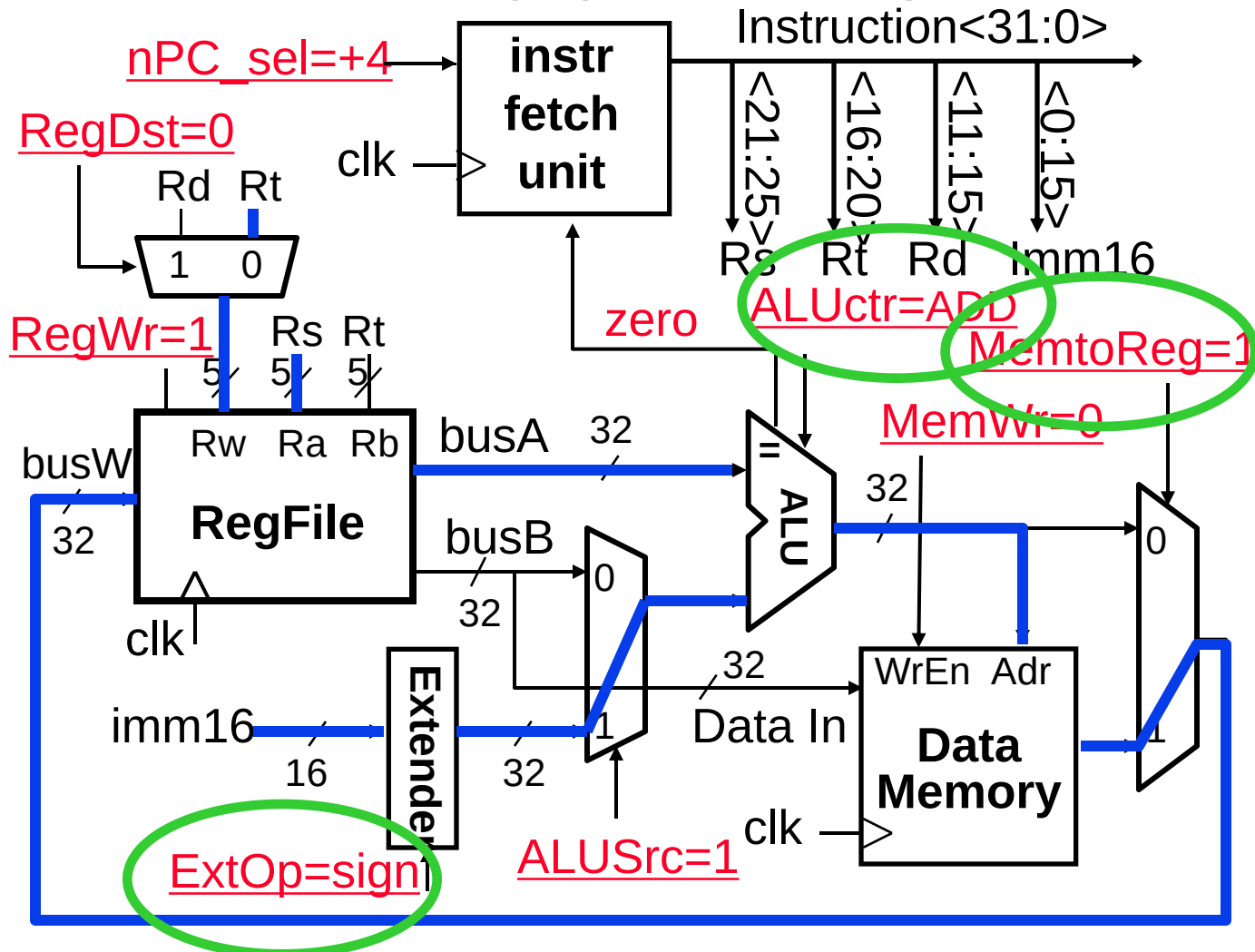
- $R[rt] = \text{Data Memory } \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Store?

 

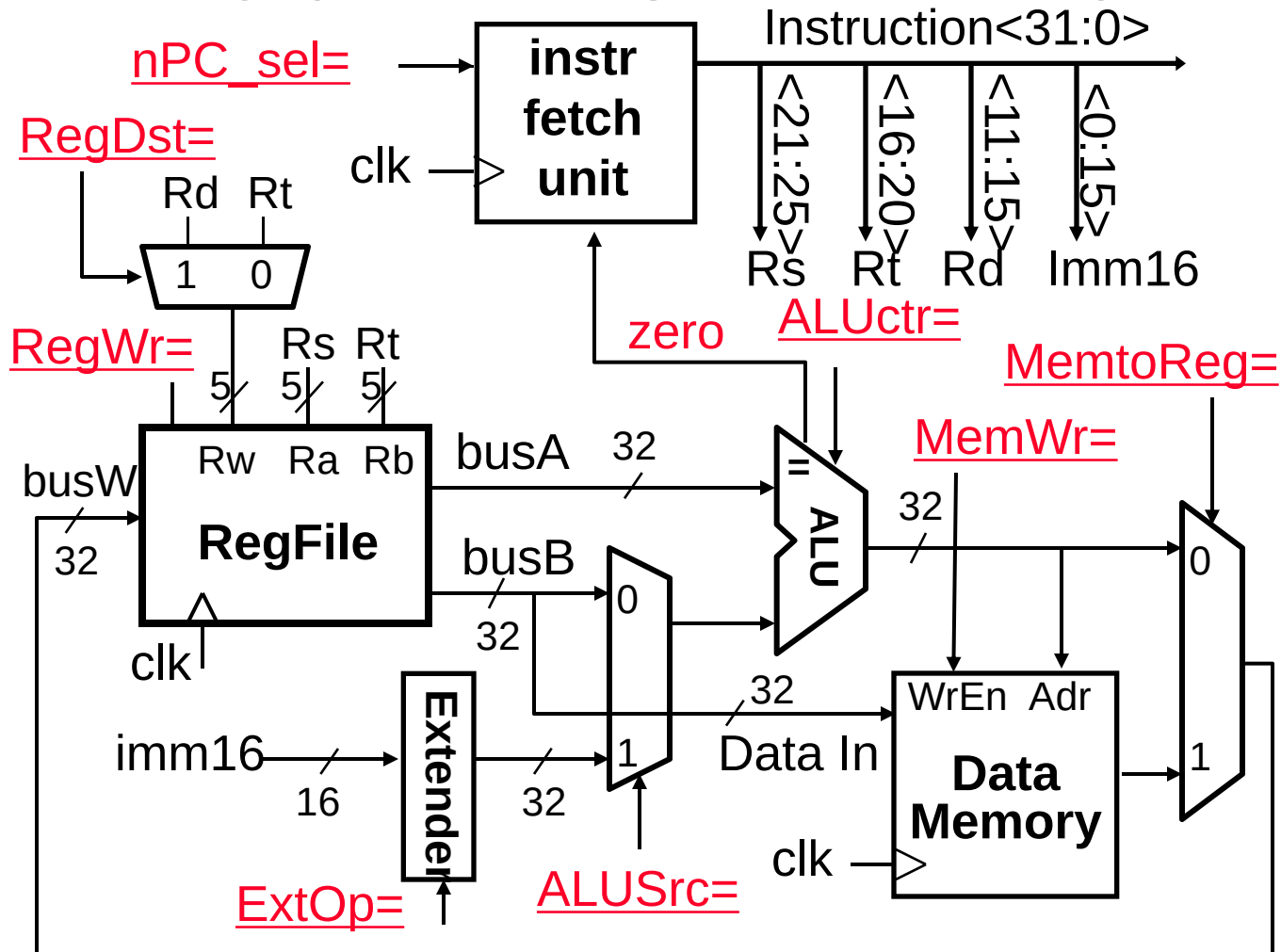
- Data Memory {R[rs] + SignExt[imm16]} = R[rt]




The Single Cycle Datapath during Store

 

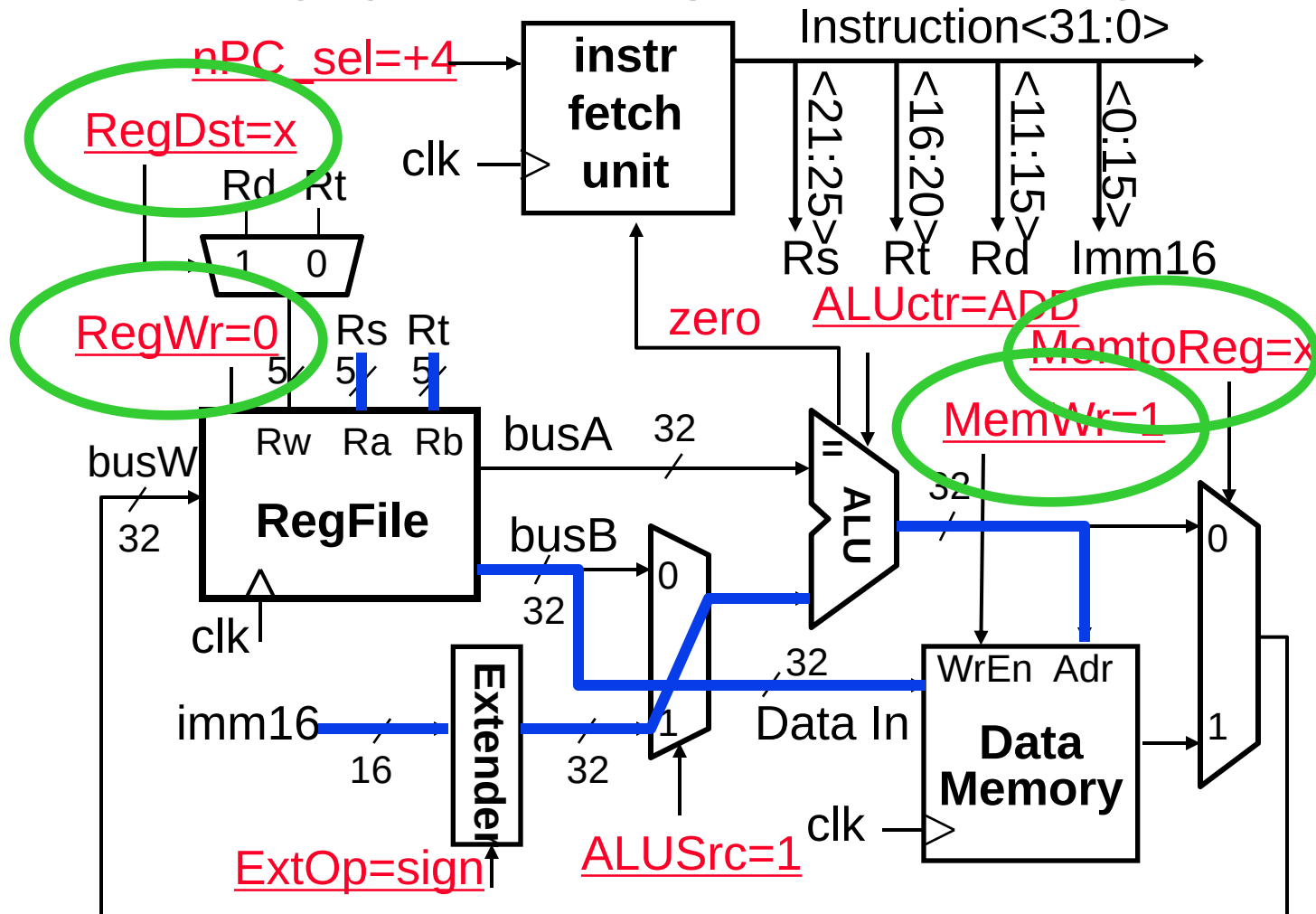
- **Data Memory {R[rs] + SignExt[imm16]} = R[rt]**




The Single Cycle Datapath during Branch?

 

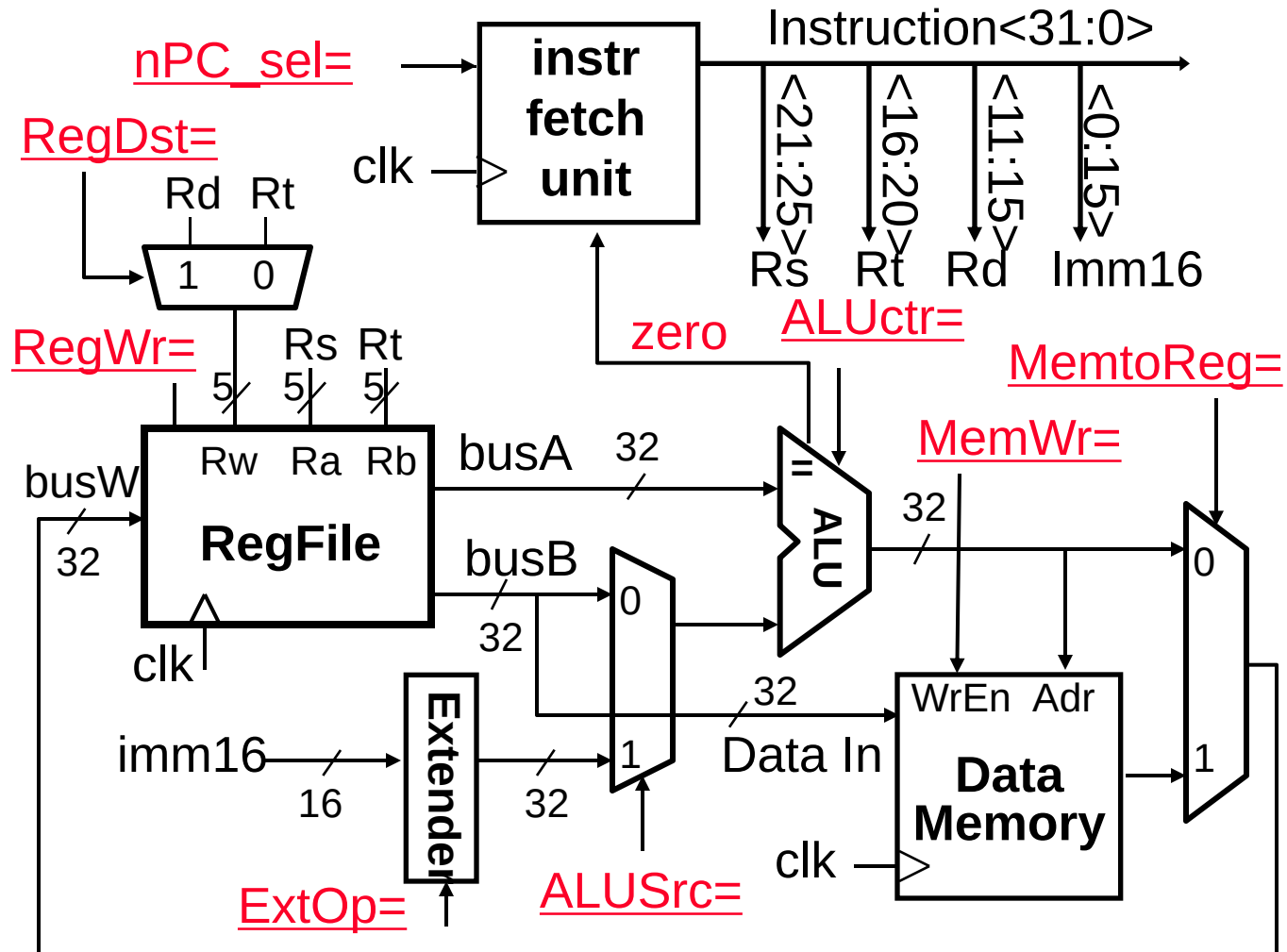
- if (R[rs] - R[rt] == 0) then Zero = 1 ; else Zero = 0




The Single Cycle Datapath during Branch

 

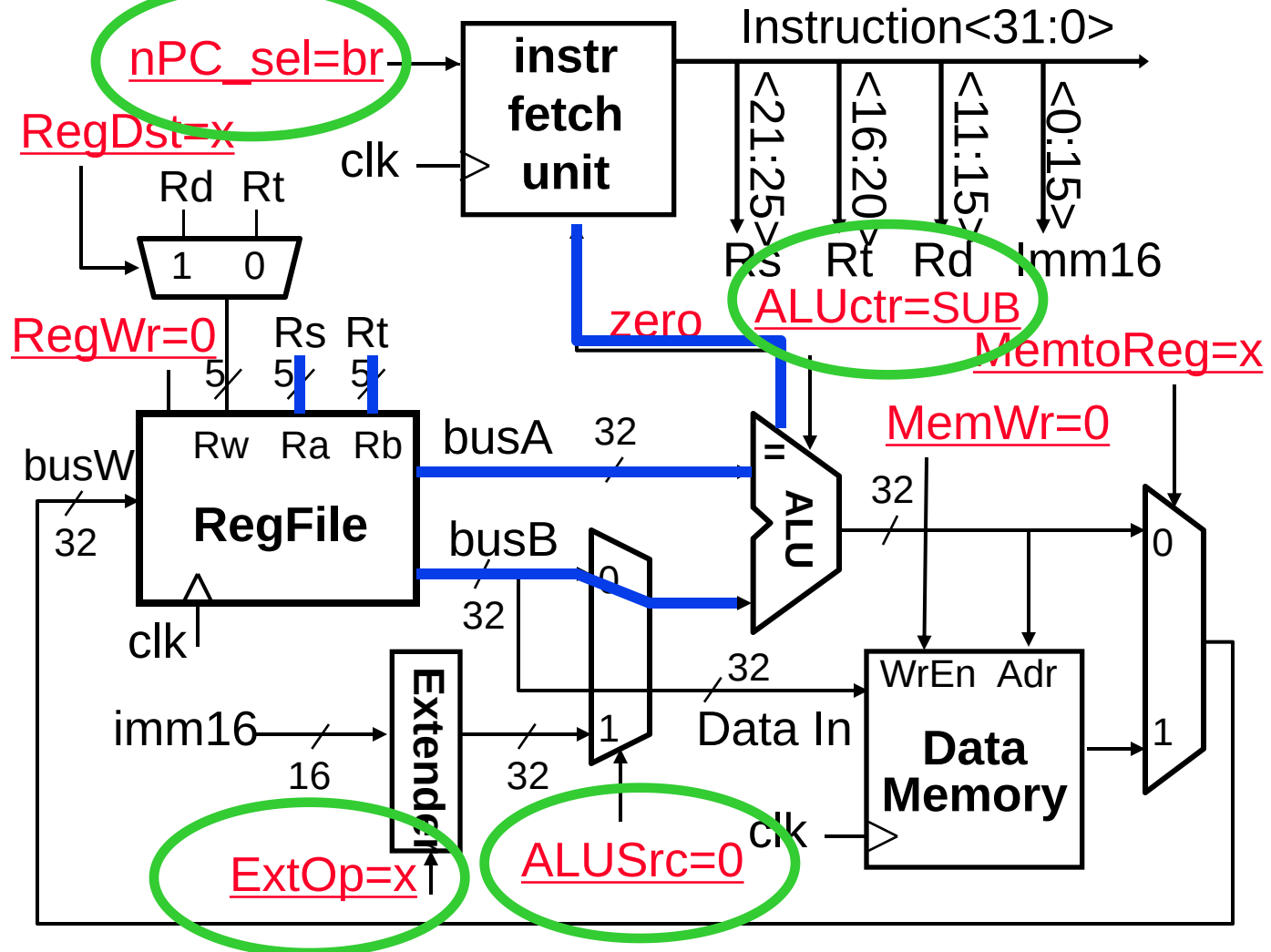
- if $(R[rs] - R[rt] == 0)$ then Zero = 1 ; else Zero = 0



 Instruction Fetch Unit at the End of Branch



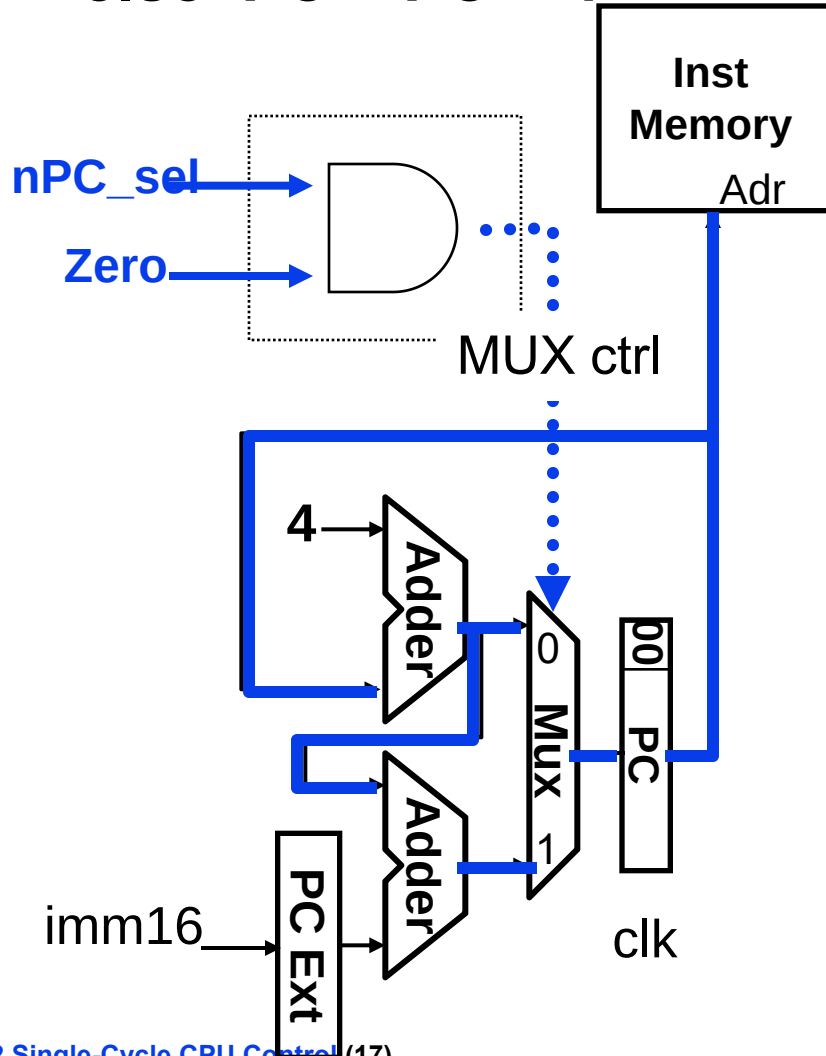- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$;
else $PC = PC + 4$



• What is encoding of nPC_sel?


- Direct MUX select?
- Branch inst. / not branch

• Let's pick 2nd option

Q: What logic gate?



Step 4: Given Datapath: RTL → Control

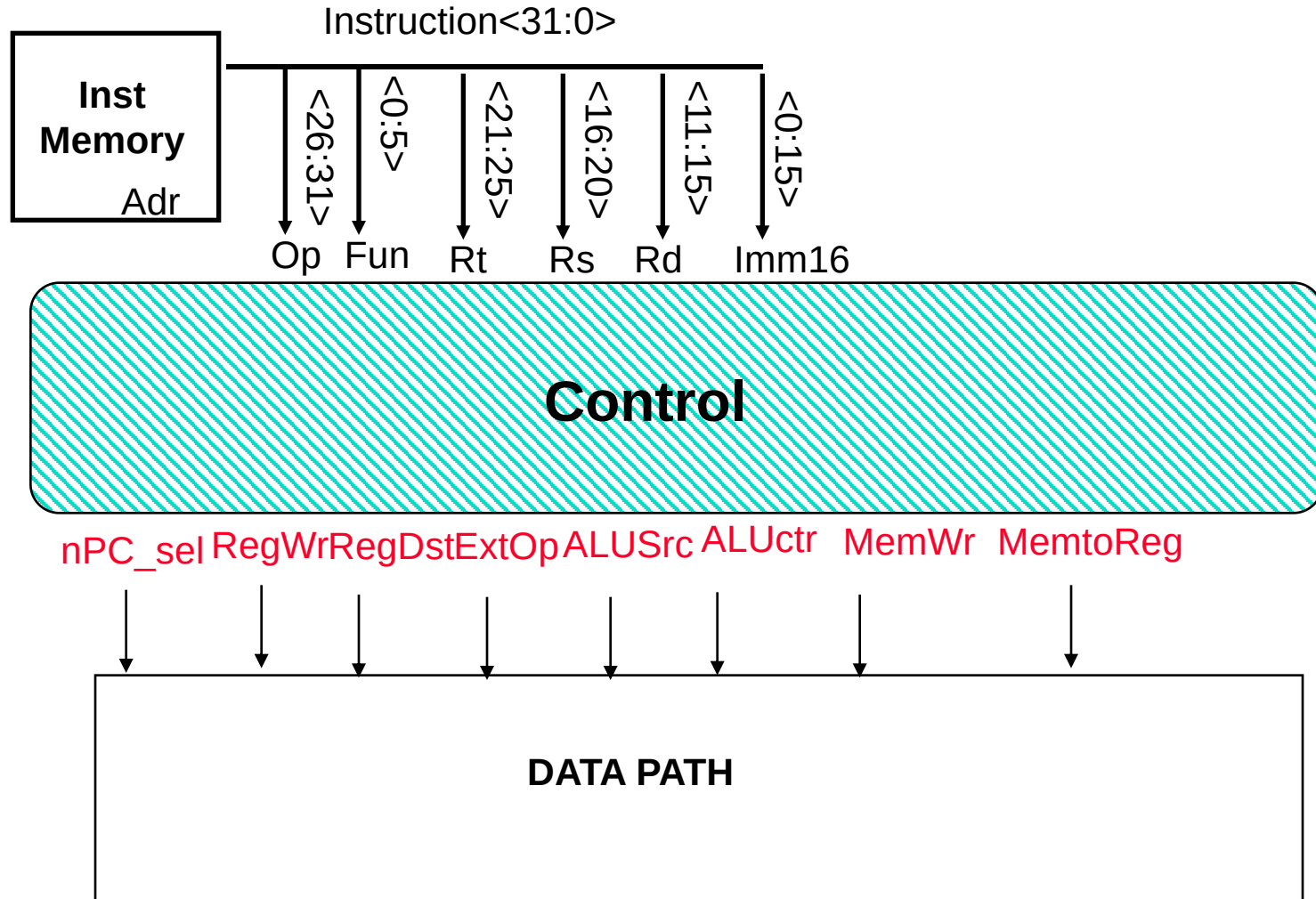

A Summary of the Control Signals (1/2)

inst Register Transfer

add $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = "ADD", RegDst = rd, RegWr, nPC_sel = "+4"

sub $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = "SUB", RegDst = rd, RegWr, nPC_sel = "+4"

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = "Z", ALUctr = "OR", RegDst = rt, RegWr, nPC_sel = "+4"

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "sn", ALUctr = "ADD", MemtoReg,
RegDst = rt, RegWr, nPC_sel = "+4"**

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$ $PC \leftarrow PC + 4$

ALUsrc = Im, Extop = "sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00$ else $PC \leftarrow PC + 4$

A Summary of the Control Signals (2/2)

See Appendix A → **func**
→ **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0101	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0						
R-type	op		rs		rt		rd		shamt		funct		add, sub
I-type	op		rs		rt		immediate						ori, lw, sw, beq
J-type	op		target address										jump

Boolean Expressions for Controller

RegDst = add + sub

ALUSrc = ori + lw + sw

MemtoReg = lw

RegWrite = add + sub + ori + lw

MemWrite = sw

nPCsel = beq

Jump = jump

ExtOp = lw + sw

ALUctr[0] = sub + beq (assume ALUctr is 00 ADD, 01: SUB, 10: OR)

ALUctr[1] = or

where,

$rtype = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet \sim op_1 \bullet \sim op_0$,

$ori = \sim op_5 \bullet \sim op_4 \bullet op_3 \bullet op_2 \bullet \sim op_1 \bullet op_0$

$lw = op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$

$sw = op_5 \bullet \sim op_4 \bullet op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$

$beq = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet op_2 \bullet \sim op_1 \bullet \sim op_0$


$jump = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet \sim op_0$

$add = rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet \sim func_1 \bullet \sim func_0$


$sub = rtype \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet func_1 \bullet \sim func_0$

How do we
implement this in
gates?

Controller Implementation

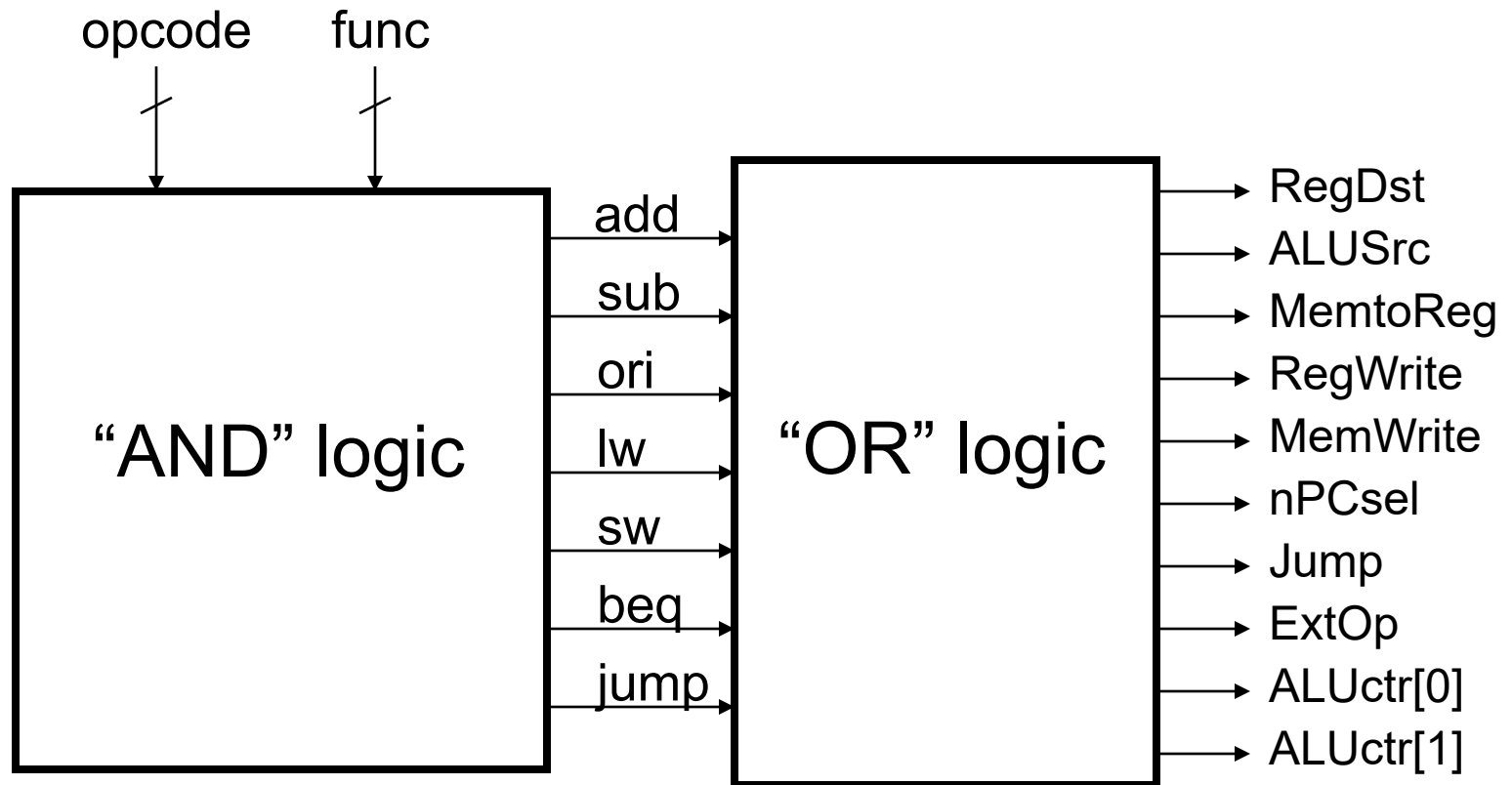

Peer Instruction

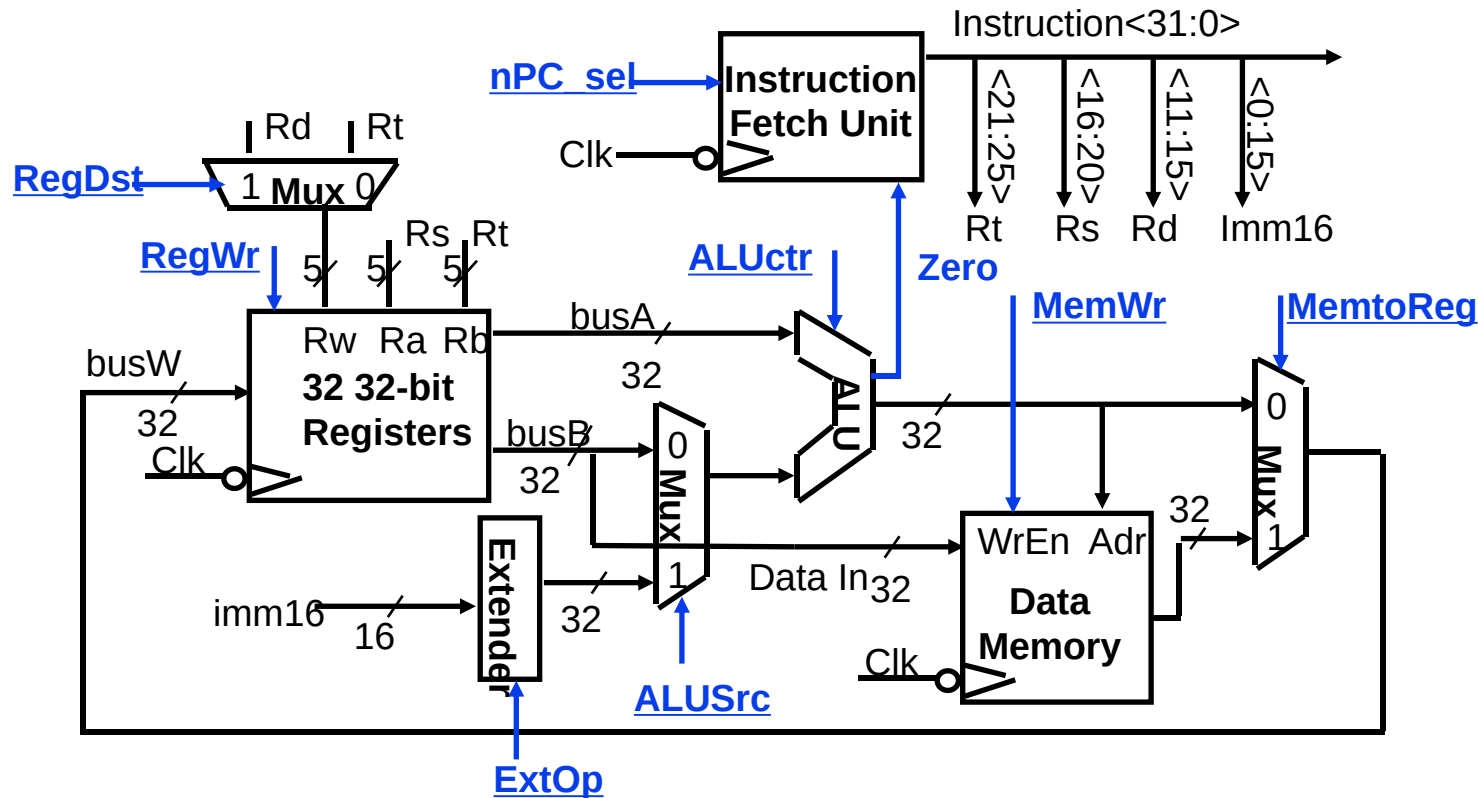


- 1) $MemToReg = 'x'$ & $ALUctr = 'sub'$.
SUB or BEQ?
- 2) $ALUctr = 'add'$. Which 1 signal is different for all 3 of: ADD, LW, & SW?
RegDst or ExtOp?

	12
a)	SR
b)	SE
c)	BR
d)	BE

Summary: Single-cycle Processor


- **5 steps to design a processor**
 - 1. Analyze instruction set → datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

 

The Single Cycle Datapath during Jump



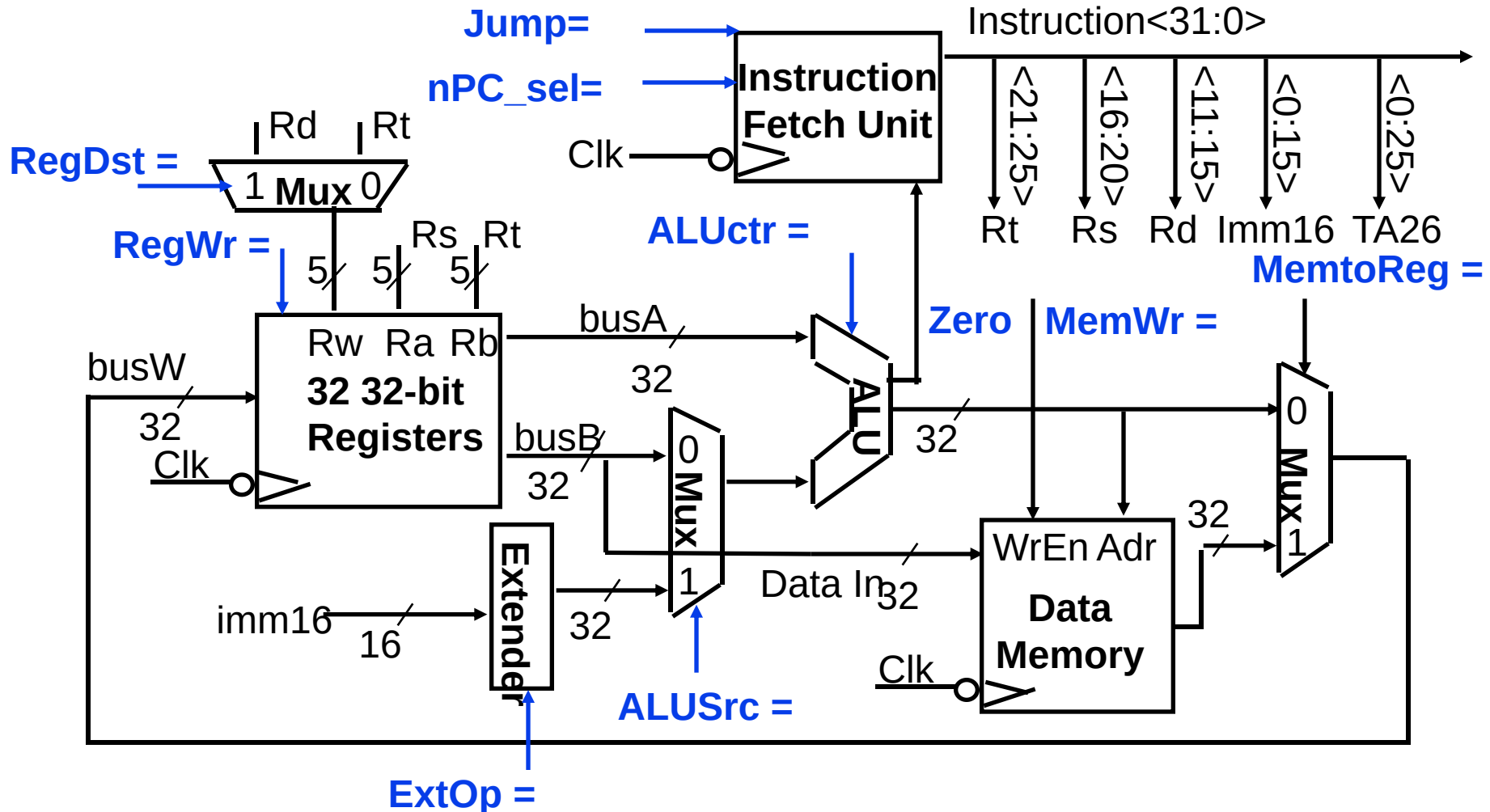
- **New PC = { PC[31..28], target address, 00 }**



The Single Cycle Datapath during Jump



 
• **New PC = { PC[31..28], target address, 00 }**



Instruction Fetch Unit at the End of Jump



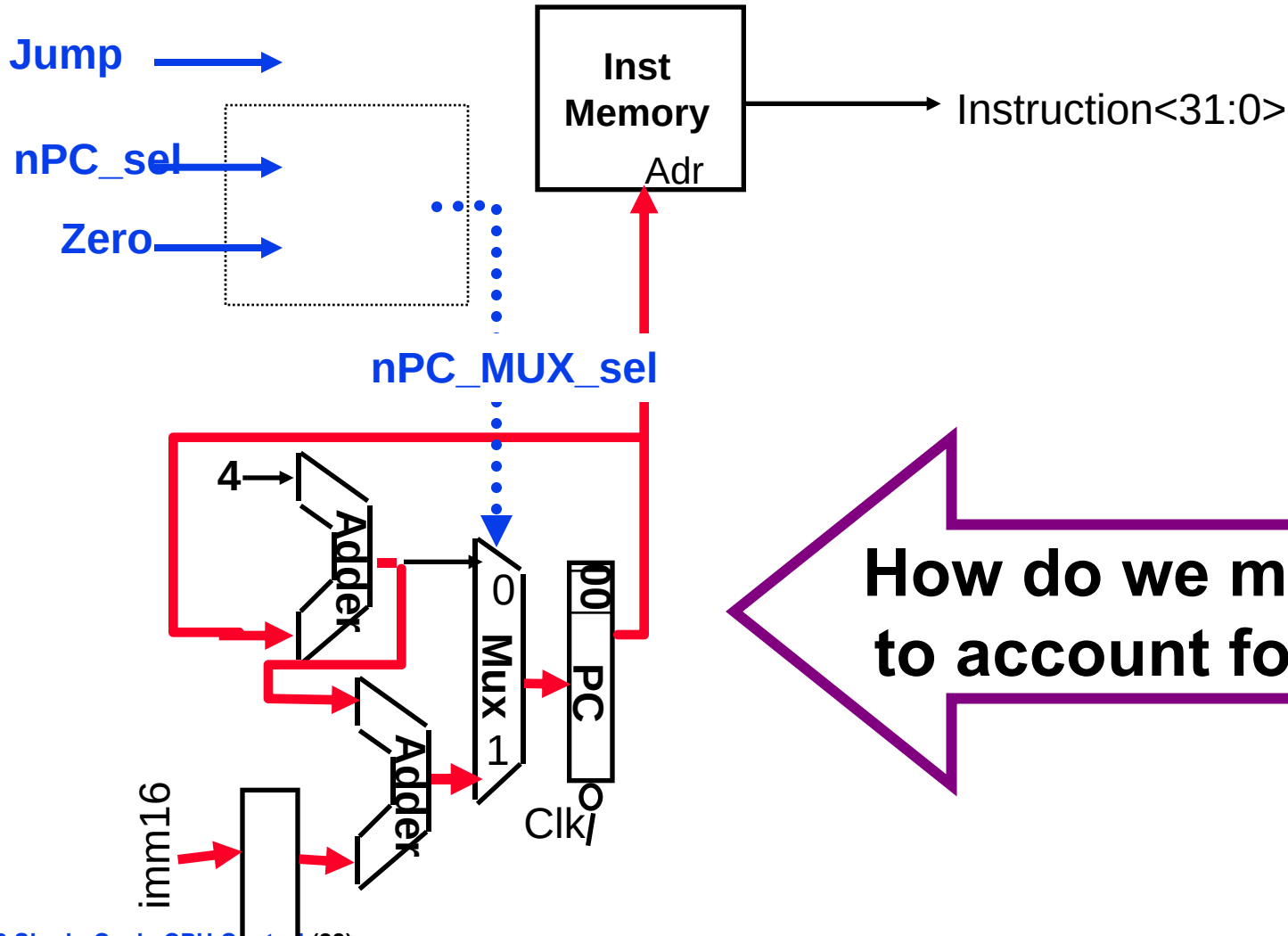- **New PC = { PC[31..28], target address, 00 }**




How do we modify this to account for jumps?

Instruction Fetch Unit at the End of Jump



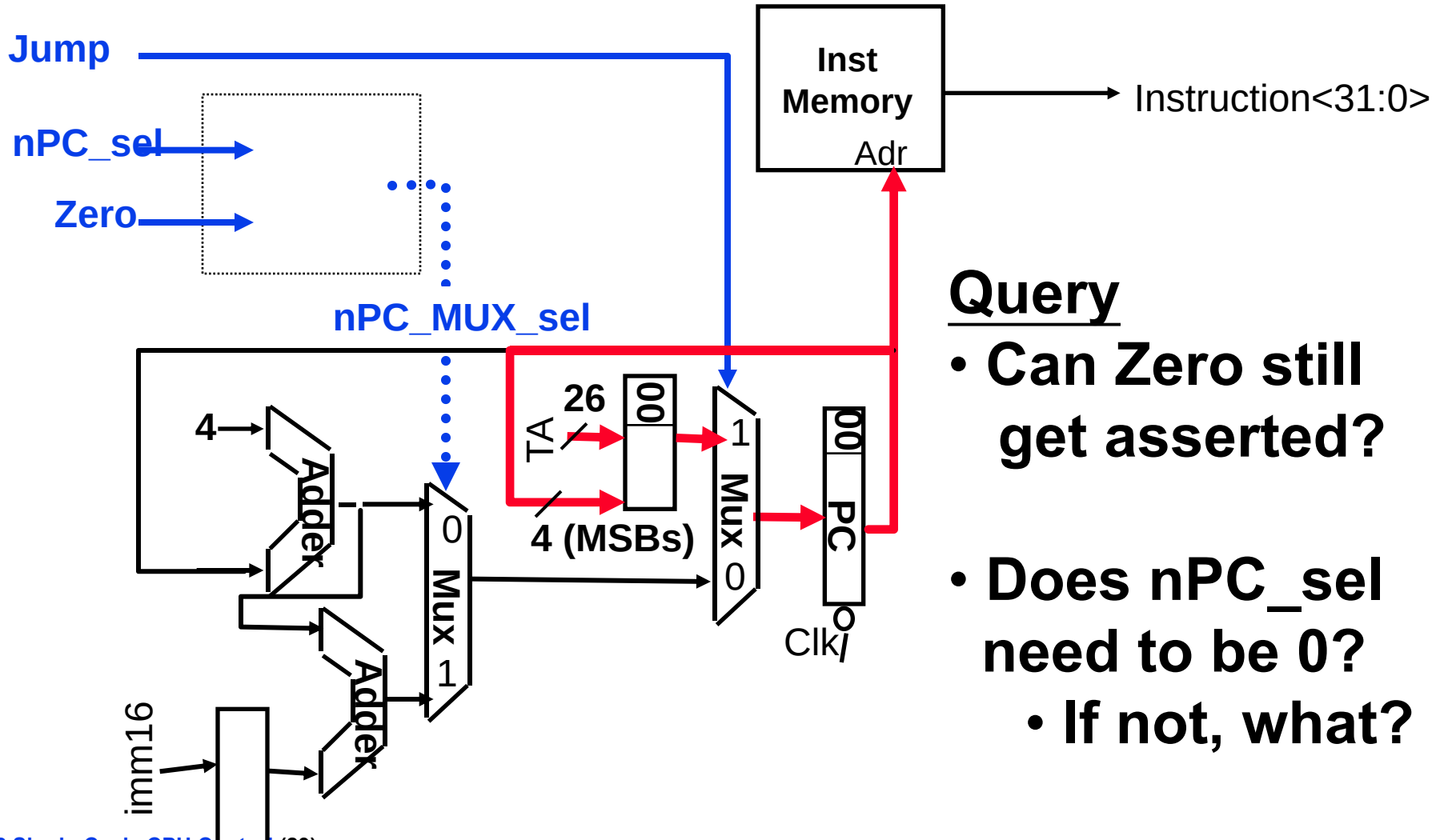• **New PC = { PC[31..28], target address, 00 }**



Query

- Can Zero still get asserted?
- Does nPC_sel need to be 0?
 - If not, what?